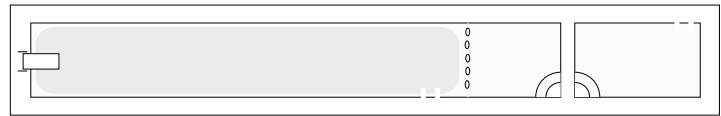


# PhyzSPRINGBOARD: PARALLEL CIRCUITS



## Electric Quantities

1. A simple circuit—such as a battery, bulb, and wire—can be characterized by the voltage, current, resistance, and power associated with it. What happens to these quantities when more and more resistors (bulbs or other electric devices) are connected to the circuit in **parallel**? Before answering, write definitions for each of the quantities.


a. Voltage / Electromotive Force

b. Current

c. Resistance

d. Power

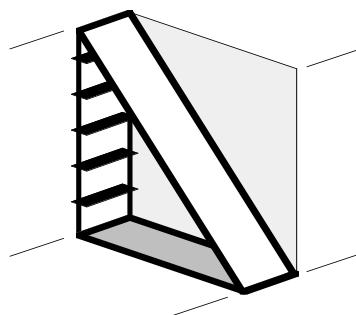2. How is each of these quantities related to characteristics of the slide?




a. The \_\_\_\_\_ of the slide is like the **resistance** of a circuit.

b. The \_\_\_\_\_ of the slide is most like the **power** of a circuit.

c. The \_\_\_\_\_ of a slide is most like the **voltage** of a circuit.

d. The \_\_\_\_\_ of a slide is most like the **current** of a circuit.

## Comparative Slidology

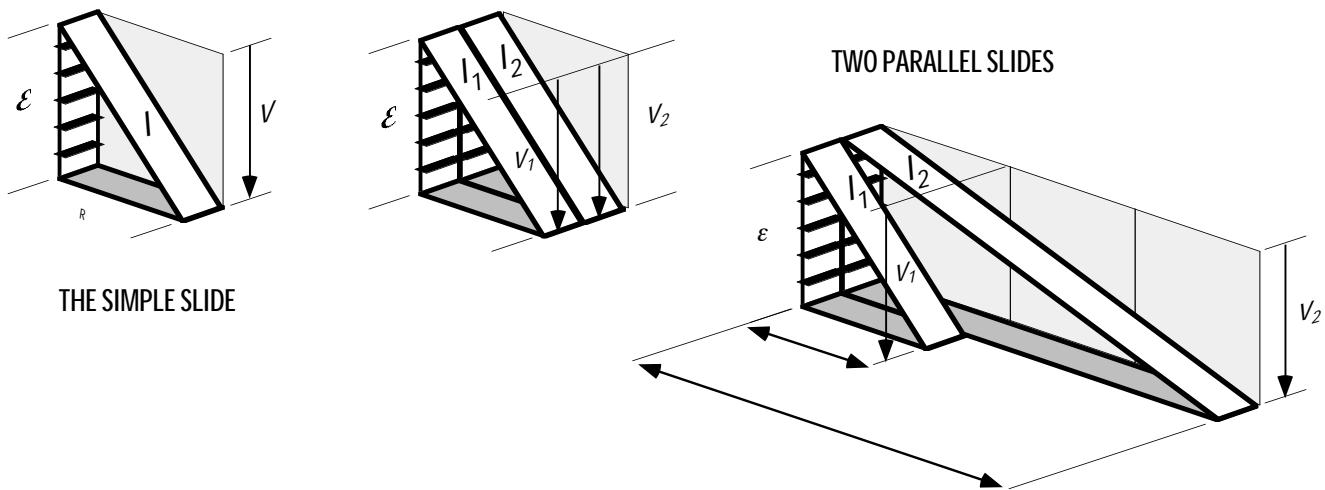

3. a. Compared to the simple slide, the elevation of a parallel slide is \_\_\_\_\_

b. Compared to the simple slide, the flow rate\* (incline) of a parallel slide is \_\_\_\_\_

\*The passenger capacity of the arrangement. For example, two identical slides can carry twice as many passengers as one.

c. Compared to the simple slide, the effective run length\*\* of a parallel slide is \_\_\_\_\_


\*\*The run length of a single, simple slide that would have the same flow rate as the parallel slide.

d. Compared to the simple slide, the bun-burning on a parallel slide is \_\_\_\_\_

4. What characteristic—if any—do both sections of a parallel slide **always** have in common?

Vertical drop     Incline     Run length     Bun-burning

## Moving on to circuits

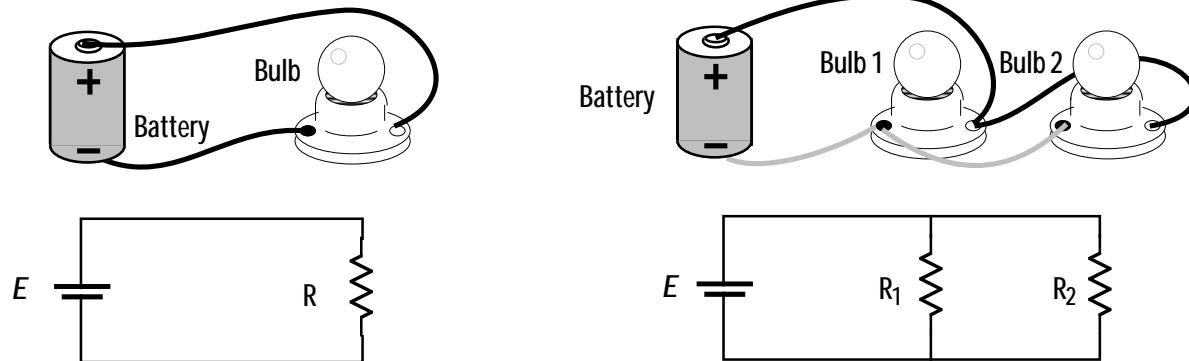

5. a. Compared to a simple circuit, the voltage of a parallel circuit is \_\_\_\_\_

b. Compared to a simple circuit, the current of a parallel circuit is \_\_\_\_\_

c. Compared to a simple circuit, the resistance of a parallel circuit is \_\_\_\_\_

d. Compared to a simple circuit, the power of a parallel circuit is \_\_\_\_\_

6. What characteristic—if any—do both resistors in a parallel circuit **always** have in common?

Voltage     Current     Resistance     Power