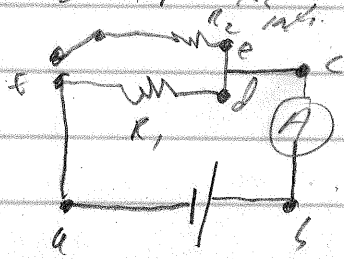


1) $V = E_{\text{mf}} - IR$ So Connected $R_{\text{int}} = \text{higher } V$



When

when switch is open
current is $a \rightarrow b \rightarrow c \rightarrow d \rightarrow f \rightarrow a$
and series through R_1 ,
so current $\Rightarrow V = IR_1$
 $I = \frac{V}{R_1}$

when switch is closed current is
 $a \rightarrow b \rightarrow c \rightarrow d \rightarrow f \rightarrow a$ so

$$I = \frac{V}{\left(\frac{1}{R_1} + \frac{1}{R_2}\right)^{-1}} \Rightarrow \text{so } R_{\text{eq}} \downarrow \text{ decreases and current increases}$$

2) First instance = 1 resistor so $V = IR$

Second instance = 2 resistors so $V = I(R_1 + R_2)$

$\frac{V}{R_1 + R_2}$ so R increases
so current
decreases

4) $V = I(R_1 + R_2)$ initially

$V = I(R_1 + R_2 + R_3)$ after adding

Current = Current = Current (Even in the battery)
increased $R = \text{decreased current}$

5) initially $V = I(R_1 + R_2)$
 adding 3rd $I = V = I(R_1 + R_2 + R_3)$

We already noted that current decreases, Resistance is constant at $(R_1 + R_2 + R_3)$

so I decreases
 R constant

So (some part) of V must decrease in order to maintain the same Voltage output the potential between the terminal must increase

6) initially $\left(\frac{1}{R_1} + \frac{1}{R_2}\right)^{-1}$


adding another $\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)^{-1}$ so resistance decreases

V = increased I
 decreased R

7) initially $\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_{\text{tot}}}$

adding 1 R $\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{R_{\text{tot}}}$

Resistance goes down
current goes down
✓

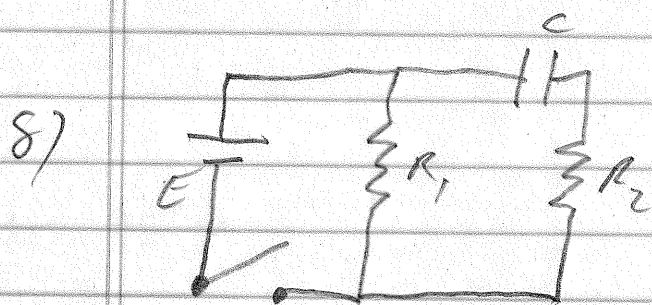

$$V = IR \quad R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \left(\frac{2}{R}\right)^{-1} = \frac{R}{2}$$

$$I = \frac{V}{R} = \frac{V}{\frac{R}{2}} = \frac{2V}{R} = \frac{2E}{R}$$

9) "after a very long time" means Cap is fully charged (Not that the battery is dead)

Battery is out of the circuit
so no current flows in the circuit